

# LAP1

## Behavioral

```
Ln#
1  LIBRARY IEEE;
2  LIBRARY WORK;
3  LIBRARY std;
4  USE IEEE.STD_LOGIC_1164.ALL;
5  USE ieee.numeric_bit.ALL;
6  USE IEEE.std_logic_arith.all;
7  USE IEEE.numeric_std.all;
8  USE IEEE.std_logic_signed.all;
9
10 ENTITY adder_sub_beh IS
11 PORT(a,b:IN std_logic_vector(3 downto 0);
12      mode:IN std_logic;
13      c_out:OUT std_logic;
14      sum :OUT std_logic_vector(3 downto 0));
15 END ENTITY adder_sub_beh;
16
17 ARCHITECTURE adder_sub_beh OF adder_sub_beh IS
18 signal result:std_logic_vector(4 downto 0);
19 BEGIN
20 M1:PROCESS(a,b,mode,result) IS
21
```

```
22 BEGIN
23 IF (mode='0') THEN
24     result<= ("0"&a) + ("0"&b);
25     sum<=result(3 downto 0);
26     c_out<=result(4);
27 ELSE
28     result<= ("0"&a) - ("0"&b);
29     sum<=result(3 downto 0);
30     c_out<=result(4);
31 END IF;
32 END PROCESS M1;
33 END ARCHITECTURE adder_sub_beh;
34
```

## Data\_flow

```
1  LIBRARY IEEE;
2  LIBRARY WORK;
3  LIBRARY std;
4  USE IEEE.std_logic_1164.ALL;
5  USE IEEE.numeric_bit.ALL;
6  USE IEEE.std_logic_arith.all;
7  USE IEEE.numeric_std.all;
8  USE IEEE.std_logic_signed.all;
9
10 ENTITY adder_sub_beh IS
11 PORT(a,b:IN std_logic_vector(3 downto 0);
12      mode:IN std_logic;
13      c_out:OUT std_logic;
14      sum :OUT std_logic_vector(3 downto 0));
15 END ENTITY adder_sub_beh;
16 ARCHITECTURE adder_sub_beh OF adder_sub_beh IS
17 signal result:std_logic_vector(4 downto 0);
18 BEGIN
19 result<=(("0"& a) + ("0"&b)) WHEN (mode='0')
20 ELSE (("0"& a) - ("0"&b));
21 sum<=result(3 downto 0);
22 c_out<=result(4);
23 END ARCHITECTURE adder_sub_beh;
24
```

---

## Structural

Ln#	
1	ENTITY full_adder IS
2	PORT(a,b,mode:IN bit;
3	c_out,sum:OUT bit);
4	END ENTITY full_adder;
5	
6	ARCHITECTURE full_adder OF full_adder IS
7	BEGIN
8	pl:process(a,b,mode) IS
9	BEGIN
10	sum<= a XOR b XOR mode;
11	c_out<=(a AND b) OR (mode AND (a XOR b));
12	END PROCESS pl;
13	
14	END ARCHITECTURE full_adder;
15	

Ln#	
1	LIBRARY IEEE;
2	LIBRARY WORK;
3	LIBRARY std;
4	USE IEEE.STD_LOGIC_1164.ALL;
5	USE ieee.numeric_bit.ALL;
6	USE IEEE.std_logic_arith.all;
7	USE IEEE.numeric_std.all;
8	USE IEEE.std_logic_signed.all;
9	
10	ENTITY adder_sub_struct IS
11	PORT(a,b:IN bit_vector(3 downto 0);
12	mode:IN bit;
13	c_out:OUT bit;
14	sum :OUT bit_vector(3 downto 0));
15	END ENTITY adder_sub_struct;
16	
17	ARCHITECTURE adder_sub_struct OF adder_sub_struct IS
18	

Ln#	
17	ARCHITECTURE adder_sub_struct OF adder_sub_struct IS
18	
19	COMPONENT add_sub_lbit IS
20	PORT (a,b,mode:IN bit;
21	c_out,sum:OUT bit);
22	END COMPONENT add_sub_lbit;
23	FOR ALL: add_sub_lbit USE ENTITY WORK.add_sub_lbit (add_sub_lbit);
24	SIGNAL carry :bit_vector(3 downto 0);
25	SIGNAL x :bit_vector(3 downto 0);
26	BEGIN
27	x(0)<=b(0) XOR mode;
28	x(1)<=b(1) XOR mode;
29	x(2)<=b(2) XOR mode;
30	x(3)<=b(3) XOR mode;
26	BEGIN
27	x(0)<=b(0) XOR mode;
28	x(1)<=b(1) XOR mode;
29	x(2)<=b(2) XOR mode;
30	x(3)<=b(3) XOR mode;
31	bit3:add_sub_lbit
32	PORT MAP(a(0),x(0) ,mode,carry(0),sum(0));
33	bit2:add_sub_lbit
34	PORT MAP(a(1),x(1) ,carry(0),carry(1),sum(1));
35	bit1:add_sub_lbit
36	PORT MAP(a(2),x(2) ,carry(1),carry(2),sum(2));
37	bit0:add_sub_lbit
38	PORT MAP(a(3),x(3) ,carry(2),carry(3),sum(3));
39	c_out<=carry(3);
40	
41	
42	END ARCHITECTURE adder_sub_struct;
43	

File Edit Format View Help

```
in1= 1100 in2= 0111 time= 10 ns out= 0011 carry= 1 mode= 0
in1= 1011 in2= 0001 time= 20 ns out= 1010 carry= 0 mode= 1
in1= 0101 in2= 0010 time= 30 ns out= 0011 carry= 0 mode= 1
```

test\_vectors.txt - Notepad

File Edit Format View Help

```
1100 0111 0
1011 0001 1
0101 0010 1
```

## Adder\_sub\_tb

```
1  USE std.textio.ALL;
2  LIBRARY IEEE;
3  LIBRARY WORK;
4  LIBRARY std;
5  USE IEEE.STD_LOGIC_1164.ALL;
6  USE ieee.numeric_bit.ALL;
7  USE IEEE.std_logic_arith.all;
8  USE IEEE.numeric_std.all;
9  USE IEEE.std_logic_signed.all;
10
11  ENTITY add_sub_tb IS
12  END ENTITY add_sub_tb ;
13
14  ARCHITECTURE add_sub_tb OF add_sub_tb IS
15
16  COMPONENT adder_sub_beh IS
17
18  PORT(a,b:IN std_logic_vector(3 downto 0);
19       mode:IN std_logic;
20       c_out:OUT std_logic;
```

```
18  PORT(a,b:IN std_logic_vector(3 downto 0);
19       mode:IN std_logic;
20       c_out:OUT std_logic;
21       sum :OUT std_logic_vector(3 downto 0));
22  END COMPONENT;
23
24  FOR dut: adder_sub_beh USE ENTITY WORK.adder_sub_beh (adder_sub_beh);
25
26  SIGNAL a,b:std_logic_vector(3 downto 0);
27  SIGNAL mode:std_logic;
28  SIGNAL sum:std_logic_vector(3 downto 0);
29  SIGNAL c_out:std_logic;
30  BEGIN
31  dut: adder_sub_beh PORT MAP(a,b,mode,c_out,sum);
32  pr: PROCESS IS
33  FILE vectors_f: text OPEN read_mode IS "E:\test_vectors.txt";
34  FILE results_f: text OPEN write_mode IS "E:\test_results.txt";
35  VARIABLE ln_file: line;
36  VARIABLE mode_t: std_logic;
```

```

35 VARIABLE ln_file: line;
36 VARIABLE mode_t: std_logic;
37 VARIABLE c_out_t: std_logic;
38 VARIABLE a_x,b_x: std_logic_vector(3 downto 0);
39 VARIABLE sum_t: std_logic_vector (3 downto 0);
40
41 VARIABLE out_file: line;
42
43 BEGIN
44 WHILE NOT endfile (vectors_f) LOOP
45 READLINE (vectors_f,ln_file);
46 READ (ln_file, a_x);
47 READ (ln_file, b_x);
48 READ (ln_file, mode_t);
49
50 -- writing variable in a,b signal
51
52 a<=a_x;
53 b<=b_x;
54 mode<=mode_t;

```

---

```

55 --now we get result
56 Wait for 10 ns;
57 c_out_t:=c_out;
58 sum_t:=sum;
59 write(out_file,string'(" in1= "));
60 write(out_file,a_x);
61 write(out_file,string'(" in2= "));
62 write(out_file,b_x);
63 write(out_file,string'(" time= "));
64 write(out_file,now);
65 write(out_file,string'(" out= "));
66 write(out_file,sum_t);
67 write(out_file,string'(" carry= "));
68 write(out_file,c_out_t);
69 write(out_file,string'(" mode= "));
70 write(out_file,mode_t);
71 writeline(results_f,out_file);

```

---

```

END LOOP;


WAIT;

END PROCESS ;

END ARCHITECTURE ;

```

---

 

File Edit Format View Help

```
in1= 1100 in2= 0111 time= 10 ns out= 0011 carry= 1 mode= 0
in1= 1011 in2= 0001 time= 20 ns out= 1010 carry= 0 mode= 1
in1= 0101 in2= 0010 time= 30 ns out= 0011 carry= 0 mode= 1
```

test\_vectors.txt - Notepad

File Edit Format View Help

```
1100 0111 0
1011 0001 1
0101 0010 1
```