

# **VHDL:**

# **Sequential Logic**

# **Modeling**

# Goals


- To understand the use of VHDL in modeling sequential logic.
- To learn the different VHDL models for finite state machines.
- To know how to model the different sequential elements: counters, parallel to serial converters, and registers.
- To learn how to model D flip-flops.
- To get familiar with flip-flop basic delay times.
- To get familiar with datapath concepts.
- To get an introduction to the concept clock skew.
- To learn how to model the different types of memories (ROMs and RAMs).

# Sequential Circuits

- The output of a **combinational circuit** depends only on the inputs.
- The output of a **sequential circuit** depends on the inputs and the **current state** of the circuit.
- A sequential value thus is able to **store** digital data in special **storage elements**.
- Sequential circuits can be classified by their function into three main types:
  1. Finite State Machines (**FSM**) or (**simple controllers**).
  2. Storage or **memory elements**.
  3. Other types of specialized circuits, such as counters, etc.
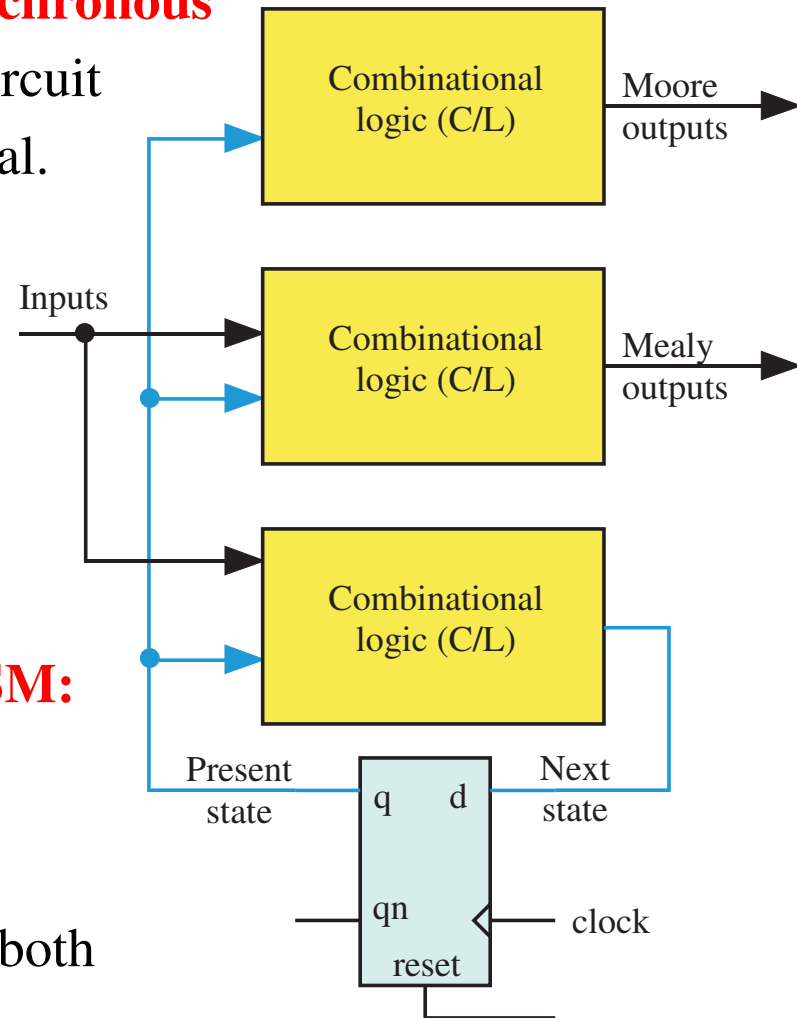
# Finite State Machines (FSMs)

- We are going to discuss only **synchronous** FSMs where all changes in the circuit occur on the edge of a clock signal.
- There are two types of FSM outputs:
  - **Moore (state-based) FSM:**  
The output depends only on the present state.
  - **Mealy (transition-based) FSM:**  
The output depends on the present state and on inputs.
- A single FSM could have one or both of these output types.



## Finite State Machines (FSMs) (Cont.)

- An FSM is described by its state diagram or state table.
- A clock input is assumed for synchronous FSM.
- A reset input is assumed for each FSM.
- Transitions between states occur **after** a clock edge when the state register is updated.
- Every state must have an outgoing transition for every input combination. As a convention, if an input combination is ignored at a certain state, it is considered a don't care input.
- Depending on the FSM type, outputs are either associated to states or transitions outgoing from them. Missing outputs should be set to zeros.

## Modeling Finite-State Machines (FSMs) (Cont.)

- Four issues must be decided upon when modeling an FSM in VHDL:
  1. Moore or Mealy type outputs
  2. VHDL coding style
  3. Resets and fail safe operation
  4. State encoding
- VHDL description of FSM requires four tasks:
  1. Asynchronous reset (RS)
  2. Update current state register (CS)
  3. Determine next state (NS)
  4. Determine outputs (OP)
- The architecture of a FSM is done using one, two, or three processes:
  - One process is not a common option.
  - It is best to model an FSM using two or three processes.

## Modeling Finite-State Machines (FSMs) (Cont.)

No. of processes		One	Two		Three		
Process No.		P 1	P 1	P 2	P 1	P 2	P 3
Tasks	RS	✓	✓		✓		
	CS	✓	✓		✓		
	NS	✓		✓		✓	
	OP	✓		✓			✓
Sensitive to	Mealy	Clock Reset CSs Inputs	Clock Reset	CSs Inputs	Clock Reset	CSs Inputs	CSs Inputs
	Moore	Clock Reset CSs	Clock Reset	CSs Inputs	Clock Reset	CSs Inputs	CSs

**Note:** Asynchronous reset.

## Modeling Finite-State Machines (FSMs) (Cont.)

- FSM must be initialized to a known state before first clock cycle.
  - Use asynchronous reset to ensure that FSM is initialized to a known state before first clock transition.
  - Asynchronous reset is modelled using IF statement.
  - Synchronous reset is modelled using IF or WAIT statements.
- Current state update could use IF or WAIT to monitor the rising edge of the clock.
- Next state logic is done using CASE statement.
- Any CASE statement must handle all possible input combinations.
- Any CASE statement must cover all possible state values to control the behavior of the state machine in unreachable states.



## FSM State Definition

- Defining the states as a new TYPE that could be declared as follows:
  1. In a PACKAGE,
  2. In an ENTITY, or
  3. In the declaration part of an ARCHITECTURE
- Defining the states as a new TYPE could be declared as:
  1. Enumerated data type,
  2. A constant representing each state, or
  3. An integer type
- State encoding can be defined by the programmer or the synthesis tool. Programmers could totally ignore state encoding.
- State encoding methods: sequential, Gray, Johnson, one-hot, etc.

## FSM State Definition (Cont.)

No.	Sequential	Gray	Johnson	One-Hot
0	0000	0000	0000_0000	0000_0000_0000_0001
1	0001	0001	0000_0001	0000_0000_0000_0010
2	0010	0011	0000_0011	0000_0000_0000_0100
3	0011	0010	0000_0111	0000_0000_0000_1000
4	0100	0110	0000_1111	0000_0000_0001_0000
5	0101	0111	0001_1111	0000_0000_0010_0000
6	0110	0101	0011_1111	0000_0000_0100_0000
7	0111	0100	0111_1111	0000_0000_1000_0000
8	1000	1100	1111_1111	0000_0001_0000_0000
9	1001	1101	1111_1110	0000_0010_0000_0000
10	1010	1111	1111_1100	0000_0100_0000_0000
11	1011	1110	1111_1000	0000_1000_0000_0000
12	1100	1010	1111_0000	0001_0000_0000_0000
13	1101	1011	1110_0000	0010_0000_0000_0000
14	1110	1001	1100_0000	0100_0000_0000_0000
15	1111	1000	1000_0000	1000_0000_0000_0000

## FSM State Definition (Cont.)

**Example: 1 (Class)** *Show how to define 8 states in a package using an enumerated data type. Use Gray encoding for states.*

```
PACKAGE enumerated_gray_encoding IS

    ATTRIBUTE enum_encoding: string;

    TYPE state IS
        (ang_0, ang_1, ang_2, ang_3, ang_4, ang_5, ang_6, ang_7);

    ATTRIBUTE enum_encoding OF state: TYPE IS
        "000 001 011 010 110 111 101 100";

END PACKAGE enumerated_gray_encoding;
```

## FSM State Definition (Cont.)

**Example: 2 (Class)** *Show how to define 8 states in a package using a constant for each state. Use Johnson state encoding for states.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

PACKAGE const_johnson_encoding IS
    CONSTANT ang_0:  unsigned (3 DOWNTO 0) := "0000";
    CONSTANT ang_1:  unsigned (3 DOWNTO 0) := "0001";
    CONSTANT ang_2:  unsigned (3 DOWNTO 0) := "0011";
    CONSTANT ang_3:  unsigned (3 DOWNTO 0) := "0111";
    CONSTANT ang_4:  unsigned (3 DOWNTO 0) := "1111";
    CONSTANT ang_5:  unsigned (3 DOWNTO 0) := "1110";
    CONSTANT ang_6:  unsigned (3 DOWNTO 0) := "1100";
    CONSTANT ang_7:  unsigned (3 DOWNTO 0) := "1000";
END PACKAGE const_johnson_encoding;
```

## Modeling Finite-State Machines (FSMs) (Cont.)

**Example: 3 (Class)** *Show how to define 8 states in a package using an integer for each state.*

```
PACKAGE integer_encoding IS
```

```
    SUBTYPE state IS integer RANGE 0 TO 7;
```



```
END PACKAGE integer_encoding;
```

# FSM Coding Style

  **Example: 4 (Class)** We want to model an odd parity checker as an FSM using VHDL.

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY fsm IS
    PORT( clk, reset: IN std_logic;
          x: IN std_logic;
          y: OUT std_logic);
END ENTITY fsm;
```



# FSM Coding Style: One Process Mealy

## Example 4: (Cont.)

```
ARCHITECTURE mealy_1p OF fsm IS
  TYPE state_type IS (even, odd);
  SIGNAL current_state: state_type;
BEGIN
  same: PROCESS (clk, reset, current_state, x) BEGIN
    IF reset = '1' THEN
      current_state <= even;
    ELSIF rising_edge (clk) THEN
      CASE current_state IS
        WHEN even =>
          IF x = '1' THEN
            current_state <= odd;
          ELSE
            current_state <= even;
          END IF;
        WHEN odd =>
          IF x = '1' THEN
            current_state <= even;
          ELSE
            current_state <= odd;
          END IF;
        WHEN OTHERS =>
          current_state <= current_state;
      END CASE;
    END IF;
  END PROCESS;
END mealy_1p;
```

## FSM Coding Style: One Process Mealy (Cont.)

### Example 4: (Cont.)

```

    :
    current_state <= odd;
  END IF;
END CASE;
END IF;
CASE current_state IS
  WHEN even =>
    IF x = '1' THEN
      y <= '1';
    ELSE
      y <= '0';
    END IF;
  WHEN odd =>
    IF x = '1' THEN
      y <= '0';
    ELSE
      y <= '1';
    END IF;
  END CASE;
END PROCESS same;
END ARCHITECTURE mealy_1p;
```



# FSM Coding Style: Two Processes Mealy

## Example 4: (Cont.)

```
ARCHITECTURE mealy_2p OF fsm IS
    TYPE state_type IS (even, odd);
    SIGNAL current_state: state_type;
    SIGNAL next_state: state_type;
BEGIN
    cs: PROCESS (clk, reset)
    BEGIN
        IF reset = '1' THEN
            current_state <= even;
        ELSIF rising_edge (clk) THEN
            current_state <= next_state;
        END IF;
    END PROCESS cs;

    :
```

## FSM Coding Style: Two Processes Mealy (Cont.)

### Example 4: (Cont.)

```

    :
    :
ns:  PROCESS (current_state, x) BEGIN
    CASE current_state IS
        WHEN even =>
            IF x = '1' THEN
                y <= '1';      next_state <= odd;
            ELSE
                y <= '0';      next_state <= even;
            END IF;
        WHEN odd =>
            IF x = '1' THEN
                y <= '0';      next_state <= even;
            ELSE
                y <= '1';      next_state <= odd;
            END IF;
        END CASE;
    END PROCESS ns;
END ARCHITECTURE mealy_2p;
```

# FSM Coding Style: Three Processes Mealy

## Example 4: (Cont.)

```
ARCHITECTURE mealy_3p OF fsm IS
    TYPE state_type IS (even, odd);
    SIGNAL current_state: state_type;
    SIGNAL next_state: state_type;
BEGIN
    cs: PROCESS (clk, reset)
    BEGIN
        IF reset = '1' THEN
            current_state <= even;
        ELSIF rising_edge (clk) THEN
            current_state <= next_state;
        END IF;
    END PROCESS cs;

    :
```

## FSM Coding Style: Three Processes Mealy (Cont.)

### Example 4: (Cont.)

```

      :
      :
ns:  PROCESS (current_state, x)
BEGIN
    CASE current_state IS
        WHEN even =>
            IF x = '1' THEN
                next_state <= odd;
            ELSE
                next_state <= even;
            END IF;
        WHEN odd =>
            IF x = '1' THEN
                next_state <= even;
            ELSE
                next_state <= odd;
            END IF;
        END CASE;
    END PROCESS ns;
      :
      :
```

## FSM Coding Style: Three Processes Mealy (Cont.)

### Example 4: (Cont.)

```

      :
      :
op:  PROCESS (current_state, x)
BEGIN
    CASE current_state IS
        WHEN even =>
            IF x = '1' THEN
                y <= '1';
            ELSE
                y <= '0';
            END IF;
        WHEN odd =>
            IF x = '1' THEN
                y <= '0';
            ELSE
                y <= '1';
            END IF;
        END CASE;
    END PROCESS OP;
END ARCHITECTURE mealy_3p;
```

# FSM Coding Style: One Process Moore

## Example 4: (Cont.)

```
ARCHITECTURE moore_1p OF fsm IS
  TYPE state_type IS (even, odd);
  SIGNAL current_state: state_type;
BEGIN
  same: PROCESS (clk, reset, current_state)
  BEGIN
    IF reset = '1' THEN
      current_state <= even;
    ELSIF rising_edge (clk) THEN
      CASE current_state IS
        WHEN even =>
          IF x = '1' THEN
            current_state <= odd;
          ELSE
            current_state <= even;
          END IF;
        :
      :
    END IF;
  END IF;
```

# FSM Coding Style: One Process Moore (Cont.)

## Example 4: (Cont.)

```

        :
        :
        WHEN odd =>
            IF x = '1' THEN
                current_state <= even;
            ELSE
                current_state <= odd;
            END IF;
        END CASE;
    END IF;
    CASE current_state IS
        WHEN even =>
            y <= '0';
        WHEN odd =>
            y <= '1';
        END CASE;
    END PROCESS same;
END ARCHITECTURE moore_1p;
```

# FSM Coding Style: Two Processes Moore

## Example 4: (Cont.)

```
ARCHITECTURE moore_2p OF fsm IS
  TYPE state_type IS (even, odd);
  SIGNAL current_state: state_type;
  SIGNAL next_state: state_type;
BEGIN
  cs: PROCESS (clk, reset)
  BEGIN
    IF reset = '1' THEN
      current_state <= even;
    ELSIF rising_edge (clk) THEN
      current_state <= next_state;
    END IF;
  END PROCESS cs;

  :
```



## FSM Coding Style: Two Processes Moore (Cont.)

### Example 4: (Cont.)

```

      ⋮
ns:  PROCESS (current_state, x)
BEGIN
    CASE current_state IS
        WHEN even =>
            y <= '0';
            IF x = '1' THEN
                next_state <= odd;
            ELSE
                next_state <= even;
            END IF;
        WHEN odd =>
            y <= '1';
            IF x = '1' THEN
                next_state <= even;
            ELSE
                next_state <= odd;
            END IF;
    END CASE;
END PROCESS ns;
END ARCHITECTURE moore_2p;
```

# FSM Coding Style: Three Processes Moore

## Example 4: (Cont.)

```
ARCHITECTURE moore_3p OF fsm IS
    TYPE state_type IS (even, odd);
    SIGNAL current_state: state_type;
    SIGNAL next_state: state_type;
BEGIN
    cs: PROCESS (clk, reset)
    BEGIN
        IF reset = '1' THEN
            current_state <= even;
        ELSIF rising_edge (clk) THEN
            current_state <= next_state;
        END IF;
    END PROCESS cs;

    :
```

## FSM Coding Style: Three Processes Moore (Cont.)

### Example 4: (Cont.)

```

      :
      :
ns:  PROCESS (current_state, x)
BEGIN
    CASE current_state IS
        WHEN even =>
            IF x = '1' THEN
                next_state <= odd;
            ELSE
                next_state <= even;
            END IF;
        WHEN odd =>
            IF x = '1' THEN
                next_state <= even;
            ELSE
                next_state <= odd;
            END IF;
        END CASE;
    END PROCESS ns;
      :
      :
```

## FSM Coding Style: Three Processes Moore (Cont.)

### Example 4: (Cont.)

```
        ⋮  
op:  PROCESS (current_state)  
BEGIN  
    CASE current_state IS  
        WHEN even =>  
            y <= '0';  
        WHEN odd =>  
            y <= '1';  
    END CASE;  
END PROCESS op;  
END ARCHITECTURE moore_3p;
```

# FSM Coding Style: Sample Testbench

## Example 4: (Cont.)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY fsm_tb IS
END ENTITY fsm_tb;
ARCHITECTURE tb_arch OF fsm_tb IS
    COMPONENT fsm IS
        PORT( clk, reset:  IN std_logic;
              x:  IN std_logic;
              y:  OUT std_logic);
    END COMPONENT fsm;
    SIGNAL clk, reset, x, y:  std_logic;
    FOR fsm_mealy_2p:  fsm USE ENTITY work.fsm (mealy_2p);
BEGIN
    clock:  PROCESS IS
    BEGIN
        clk <= '0', '1' AFTER 10 ns;
        WAIT FOR 20 ns;
    END PROCESS clock;

    :
```

# FSM Coding Style: Sample Testbench (Cont.)

## Example 4: (Cont.)

```

      :
sg:  PROCESS IS
BEGIN
    reset <= '1';
    WAIT FOR 10 ns;
    ASSERT y = '0'
        REPORT "Error:  Reset"
        SEVERITY warning;
    reset <= '0';  x <= '0';
    WAIT FOR 10 ns;
    ASSERT y = '0'
        REPORT "Error:  state even when x = 0"
        SEVERITY warning;
    WAIT FOR 10 ns;
    x <= '1';
    WAIT FOR 10 ns;
    ASSERT y = '1'
        REPORT "Error:  state even when x = 1"
        SEVERITY warning;
    :

```


# FSM Coding Style: Sample Testbench (Cont.)

## Example 4: (Cont.)

```
        :  
WAIT FOR 10 ns;  
x <= '0';  
WAIT FOR 10 ns;  
ASSERT y = '1'  
    REPORT "Error:  state odd when x = 0"  
    SEVERITY warning;  
WAIT FOR 10 ns;  
x <= '1';  
WAIT FOR 10 ns;  
ASSERT y = '0'  
    REPORT "Error:  state odd when x = 1"  
    SEVERITY warning;  
WAIT;  
END PROCESS sg;  
fsm_mealy_2p: fsm PORT MAP (clk, reset, x, y);  
END ARCHITECTURE tb_arch;
```

# FSM Coding Style: Sample Output


## Example 4: (Cont.)

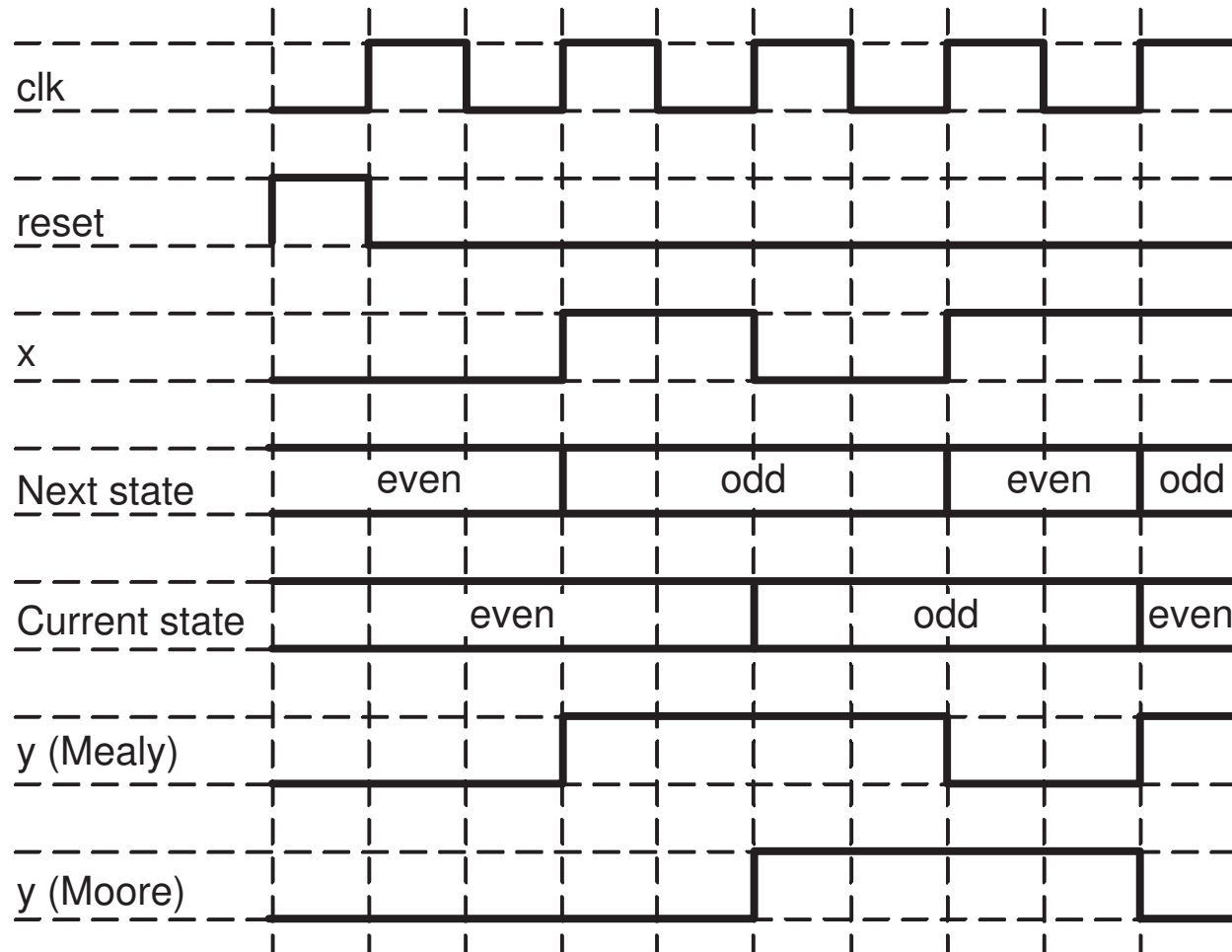



## Modeling Finite-State Machines (FSMs) (Cont.)

 **Example: 5 (Class)** *Encode the shown FSM using VHDL. The machine has a synchronous reset input. Use Johnson state encoding for states through the previously defined package. Use a three-process coding style.*



# Modeling Finite-State Machines (FSMs) (Cont.)

## Example 5: (Cont.)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
USE work.const_johnson_encoding.ALL;
ENTITY angle IS
    PORT( clk, reset, cw, ccw:  IN std_logic;
          angle:  OUT std_logic_vector (2 DOWNTO 0));
END ENTITY angle;
ARCHITECTURE angle OF angle IS
    SIGNAL current_state, next_state:  unsigned (3 DOWNTO 0);
BEGIN -- states have same number of bits as the encoding of ang_0, etc.
    cs:  PROCESS IS BEGIN
        WAIT UNTIL rising_edge (clk);
        IF reset = '1' THEN -- synchronous reset
            current_state <= ang_0;
        ELSE
            current_state <= next_state;
        END IF;
    END PROCESS cs;

    :
```

# Modeling Finite-State Machines (FSMs) (Cont.)

## Example 5: (Cont.)

```

      ⋮
ns:  PROCESS (current_state, cw, ccw) IS BEGIN
      CASE current_state IS
        WHEN ang_0 =>
          IF cw = '1' AND ccw = '0' THEN
            next_state <= ang_1;
          ELSIF cw = '0' AND ccw = '1' THEN
            next_state <= ang_7;
          ELSE
            next_state <= ang_0;
          END IF;
        WHEN ang_1 =>
          IF cw = '1' AND ccw = '0' THEN
            next_state <= ang_2;
          ELSIF cw = '0' AND ccw = '1' THEN
            next_state <= ang_0;
          ELSE
            next_state <= ang_1;
          END IF;
      ⋮

```

# Modeling Finite-State Machines (FSMs) (Cont.)

## Example 5: (Cont.)

```

        :
        :
    WHEN ang_7 =>
        IF cw = '1' AND ccw = '0' THEN
            next_state <= ang_0;
        ELSIF cw = '0' AND ccw = '1' THEN
            next_state <= ang_6;
        ELSE
            next_state <= ang_7;
        END IF;
    WHEN OTHERS =>
        next_state <= ang_0;
    END CASE;
END PROCESS ns;

    :
    :
```

# Modeling Finite-State Machines (FSMs) (Cont.)

## Example 5: (Cont.)

```

      :
      :
op:  PROCESS (current_state) IS
BEGIN
    CASE current_state IS
        WHEN ang_0  => angle <= o"0";
        WHEN ang_1  => angle <= o"1";
        WHEN ang_2  => angle <= o"2";
        WHEN ang_3  => angle <= o"3";
        WHEN ang_4  => angle <= o"4";
        WHEN ang_5  => angle <= o"5";
        WHEN ang_6  => angle <= o"6";
        WHEN ang_7  => angle <= o"7";
        WHEN OTHERS => NULL;
    END CASE;
END PROCESS op;
END ARCHITECTURE angle;
```

# Counters

**Example: 6 (Class)** *Model an n-bit binary up/down counter with synchronous clear and preset.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY bin_counter IS
    GENERIC( n:  positive := 4);
    PORT( clk, clear, preset, up_down:  IN std_logic;
          d_in:  IN unsigned (n-1 DOWNT0 0);
          d_out:  OUT unsigned (n-1 DOWNT0 0));
END ENTITY bin_counter;

ARCHITECTURE behav OF bin_counter IS
    SIGNAL counter:  unsigned (n-1 DOWNT0 0);
BEGIN

    :
```

## Counters (Cont.)

### Example 6: (Cont.)

```

      ⋮
ct:  PROCESS (clk) IS BEGIN
    IF rising_edge (clk) THEN
        IF clear = '1' THEN
            counter <= (OTHERS => '0');
        ELSIF preset = '1' THEN
            counter <= d_in;
        ELSIF up_down = '1' THEN
            counter <= counter + 1;
        ELSE
            counter <= counter - 1;
        END IF;
    END IF;
END PROCESS ct;
d_out <= counter;
END ARCHITECTURE behav;
```

## Counters (Cont.)

**Example: 7 (Class)** *Model an n-bit Gray up/down counter with synchronous clear.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY gray_counter IS
    GENERIC( n:  positive := 4);
    PORT( clk, clear, up_down:  IN std_logic;
          dout:  OUT std_logic_vector (n-1 DOWNT0 0));
END ENTITY gray_counter;

ARCHITECTURE behav OF gray_counter IS
    COMPONENT bin_counter IS
        GENERIC( n:  positive := 4);
        PORT( clk, clear, up_down:  IN std_logic;
              preset:  IN std_logic;
              d_in:  IN unsigned (n-1 DOWNT0 0) := (OTHERS => '0');
              dout:  OUT unsigned (n-1 DOWNT0 0));
    END COMPONENT bin_counter;

    :
```



## Counters (Cont.)

### Example 7: (Cont.)

```

      ⋮
FOR ALL: bin_counter USE ENTITY WORK.bin_counter (behav);

SIGNAL d_bin:  unsigned (n-1 DOWNTO 0);
BEGIN
  bcount:  bin_counter GENERIC MAP ( n => 4)
            PORT MAP (   clk => clk, clear => clear
                        up_down => up_down, preset => '0',
                        d_in => OPEN, d_out => d_bin);

  gray:  PROCESS (d_bin) IS
  BEGIN
    d_out(n-1) <= d_bin(n-1);
    FOR j IN n-2 DOWNTO 0 LOOP
      d_out(j) <= d_bin (j+1) XOR d_bin (j);
    END LOOP;
  END PROCESS gray;
END ARCHITECTURE behav;
```

**Notice that if an input port is to be left open, a default value must be specified for it.**

# Parallel to Serial Converter


**Example: 8 (Class)** *A parallel to serial converter that scans out the MSB first.*

```
ENTITY p2s IS
    GENERIC( n:  positive := 4);
    PORT( d_in:  IN bit_vector (0 TO n-1);
          clk, load, shift:  IN bit;
          d_out:  OUT bit);
END ENTITY p2s;
ARCHITECTURE shift OF p2s IS
    SIGNAL save:  bit_vector (0 TO n-1);
BEGIN
    ps:  PROCESS (clk) IS BEGIN
        IF clk = '1' AND clk'event THEN
            IF load = '1' THEN
                save <= d_in;
            ELSIF shift = '1' THEN
                save <= save (1 TO n-1) & '0';
            END IF;
        END IF;
    END PROCESS ps;
    d_out <= save(0);
END ARCHITECTURE shift;
```

# Flip-Flops

 **Example: 9 (Class)** *Model a negative edge-triggered D flip-flop with select input.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY d_ff_sel IS
    PORT( d1, d0, sd, clk: IN std_logic;
          q, qn: OUT std_logic);
END ENTITY d_ff_sel;
ARCHITECTURE sel OF d_ff_sel IS
BEGIN
    s1: PROCESS IS
    BEGIN
        WAIT UNTIL falling_edge (clk);
        IF sd = '1' THEN
            q <= d1;          qn <= NOT d1;
        ELSE
            q <= d0;          qn <= NOT d0;
        END IF;
    END PROCESS s1;
END ARCHITECTURE sel;
```



## Flip-Flops (Cont.)

**Example: 10 (Class)** *Model a positive edge-triggered D flip-flop with asynchronous clear and set.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY d_ff_async IS
    PORT( clk, clear, set: IN std_logic;
          d_in: IN std_logic;
          d_out: OUT std_logic);
END ENTITY d_ff_async;
ARCHITECTURE async OF d_ff_async IS BEGIN
    asr: PROCESS (clk, clear, set) IS BEGIN
        IF clear = '1' THEN
            d_out <= '0';
        ELSIF set = '1' THEN
            d_out <= '1';
        ELSIF rising_edge (clk) THEN
            d_out <= d_in;
        END IF;
    END PROCESS asr;
END ARCHITECTURE async;
```


## Flip-Flops (Cont.)

**Example: 11 (Class)** *Repeat Example 10 with synchronous clear and set.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY d_ff_sync IS
    PORT( clk, clear, set:  IN std_logic;
          d_in:  IN std_logic;
          d_out:  OUT std_logic);
END ENTITY d_ff_sync;
ARCHITECTURE sync OF d_ff_sync IS BEGIN
    ssr:  PROCESS IS BEGIN
        WAIT UNTIL rising_edge (clk);
        IF clear = '1' THEN
            d_out <= '0';
        ELSIF set = '1' THEN
            d_out <= '1';
        ELSE
            d_out <= d_in;
        END IF;
    END PROCESS ssr;
END ARCHITECTURE sync;
```

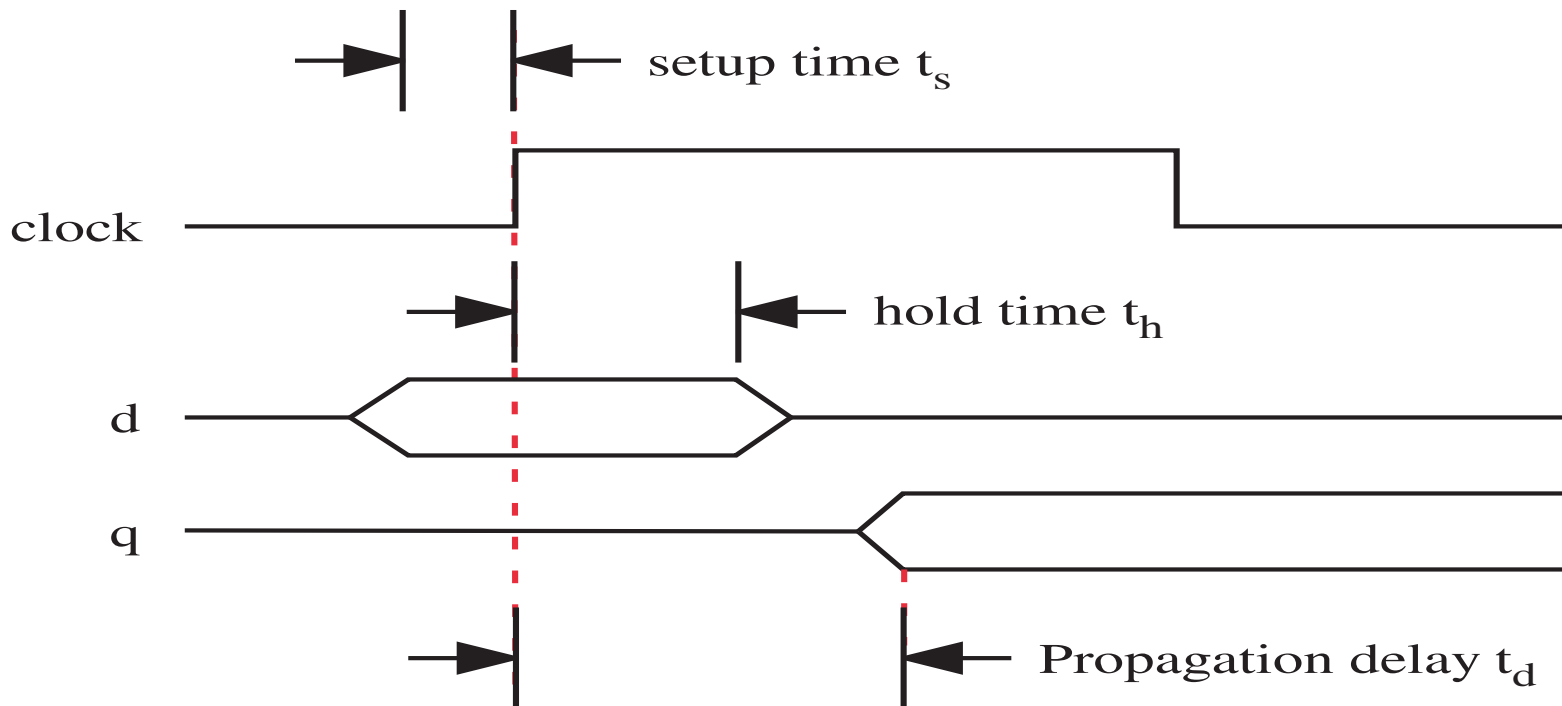
## Flip-Flops (Cont.)

- **Setup time  $t_s$** : Minimum time during which data must be stable prior to a clock edge.
- **Hold time  $t_h$** : Minimum time during which input data must be stable after a clock edge. You cannot sample output data during this time. Hold times are usually either 0 or very small.


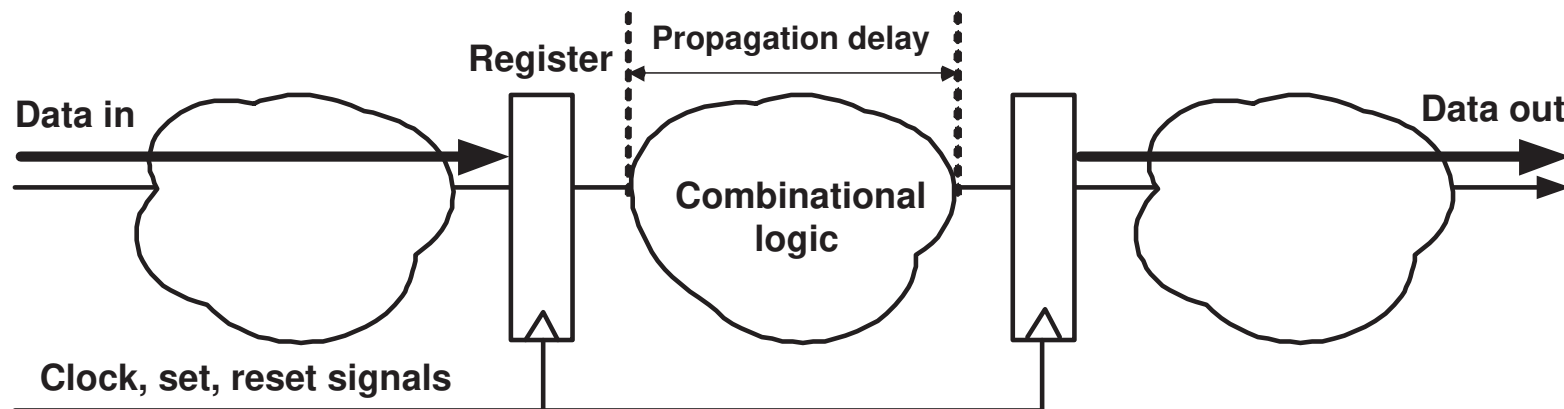
## Flip-Flops (Cont.)

- **Propagation delay  $t_d$ :** Time to produce correct result of the circuit measured from the clock edge.
- **Clock skew  $T_{cs}$ :** Arrival of a clock signal at the clock inputs of different flip-flops at different times as a result of propagation delays.
- Given two adjacent flip-flops,  $i$  and  $j$ , the clock skew between them ( $T_{cs_{i,j}}$ ) is defined as  $T_{cs_{i,j}} = T_{cs_i} - T_{cs_j}$ , where  $T_{cs_i}$  and  $T_{cs_j}$  are the clock delays from the clock source to  $i$  and  $j$ , respectively.



$$\text{Clock period} \geq t_d + \text{combinational logic propagation delay} + t_s + 2 \times T_{cs}$$

## Flip-Flops (Cont.)

**Example: 12 (Class)** *Model a D flip-flop with setup, hold, and delay times.*

```
ENTITY d_ff IS
    GENERIC( setup, hold:  time := 0.1 ns; delay:  time := 2 ns);
    PORT( d, clk:  IN bit;
          q:  OUT bit);
END ENTITY d_ff;

ARCHITECTURE d_ff OF d_ff IS BEGIN
    q <= d AFTER delay WHEN clk = '1' AND clk'event;
    check_setup:  PROCESS IS BEGIN
        WAIT UNTIL clk = '1' AND clk'event;
        ASSERT d'last_event >= setup      -- Same as d'stable (setup)
            REPORT "setup violation"
            SEVERITY warning;
    END PROCESS check_setup;
    check_hold:  PROCESS IS BEGIN
        WAIT UNTIL clk'delayed (hold) = '1' AND clk'delayed (hold)'EVENT;
        ASSERT d'stable (hold)          -- Same as d'last_event >= hold
            REPORT "hold violation"
            SEVERITY warning;
    END PROCESS check_hold;
END ARCHITECTURE d_ff;
```



## Flip-Flops (Cont.)

### Example 12: (Cont.)

```
ENTITY dff_test IS
END ENTITY dff_test;
ARCHITECTURE test OF dff_test IS
    COMPONENT d_ff IS
        GENERIC(
            delay: time := 4 ns;
            setup: time := 3 ns;
            hold:  time := 1 ns);
        PORT(
            d, clk: IN bit;
            q:  OUT bit);
    END COMPONENT d_ff;
    FOR gate: d_ff USE ENTITY WORK.d_ff (basic);
    SIGNAL d_in, clock, d_out: bit;
BEGIN
    gate: d_ff    GENERIC MAP(
                        delay => 4 ns,
                        setup => 3 ns,
                        hold  => 1 ns)
                        PORT MAP(
                            d => d_in,
                            clk => clock,
                            q => d_out);
END ARCHITECTURE test;
```

# Registers

**Example: 13 (Class)** *Model a shift register to perform the operations in the table below. A zero asynchronous clr signal resets all output bits.*

Function	Control inputs (s1, s0)	q[3]	q[2]	q[1]	q[0]
Hold value	0 0	q[3]	q[2]	q[1]	q[0]
Shift left	0 1	q[2]	q[1]	q[0]	r_in
Shift right	1 0	l_in	q[3]	q[2]	q[1]
Load	1 1	d[3]	d[2]	d[1]	d[0]

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY sr IS
    GENERIC( width:  positive := 4);
    PORT( clk, clr, l_in, r_in, s0, s1:  IN std_logic;
          d:  IN std_logic_vector (width-1 DOWNTO 0);
          q:  INOUT std_logic_vector (width-1 DOWNTO 0));
END ENTITY sr;

:
:

```

## Registers (Cont.)

### Example 13: (Cont.)

```

      ⋮
ARCHITECTURE sr OF sr IS
BEGIN
    shift: PROCESS (clk, clr) IS
        VARIABLE sel: std_logic_vector (1 DOWNTO 0);
    BEGIN
        IF clr = '0' THEN
            q <= (OTHERS => '0');
        ELSIF rising_edge (clk) THEN
            sel := s1 & s0;
            CASE sel IS
                WHEN "00" => NULL;
                WHEN "01" => q <= q(width-2 DOWNTO 0) & r_in;
                WHEN "10" => q <= l_in & q(width-1 DOWNTO 1);
                WHEN "11" => q <= d;
                WHEN OTHERS => NULL;
            END CASE;
        END IF;
    END PROCESS shift;
END ARCHITECTURE sr;
```

# ROMs

**Example: 14 (Class)** *Show how to use a ROM component that was designed using standard cells.*

```

      :
      :
COMPONENT ROM IS
  PORT(  en:  IN std_logic;
         address:  IN unsigned (m-1 DOWNT0 0);
         q:  OUT std_logic_vector (n-1 DOWNT0 0));
END COMPONENT ROM;
SIGNAL enable:  std_logic;
SIGNAL address_bus:  unsigned (m-1 DOWNT0 0);
SIGNAL data_bus:  std_logic_vector (n-1 DOWNT0 0);
BEGIN
  r1:  ROM( en => enable, address => address_bus, q => data_bus);
      :
      :

```

## ROMs (Cont.)

**Example: 15 (Class)** *Use a ROM to build a squaring circuit. Use a flag to ensure that the ROM is initialize only one time.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY rom IS
    GENERIC( n: integer := 3;
             m: integer := 6);
    PORT( enable: IN std_logic;
          address: IN unsigned (n-1 DOWNT0 0);
          data: OUT unsigned (m-1 DOWNT0 0));
END ENTITY rom;

:
```

## Example 15: (Cont.)

## ROMs (Cont.)

```

      ⋮
ARCHITECTURE flag_arch OF rom IS
    TYPE rm IS ARRAY (0 TO 2**n-1) OF unsigned (m-1 DOWNT0 0);
    SIGNAL word:  rm;
    SIGNAL initialized:  boolean := false;
BEGIN
    memory:  PROCESS (enable, address) IS BEGIN
        IF NOT initialized THEN
            FOR index IN word'range LOOP
                word(index) <= to_unsigned(index*index, m);
            END LOOP;
            ASSERT FALSE REPORT "ROM init in flag_arch" SEVERITY note;
            initialized <= true;
        END IF;
        IF enable = '1' THEN
            data <= word(to_integer(address));
        ELSE
            data <= (OTHERS => 'Z');
        END IF;
    END PROCESS memory;
END ARCHITECTURE flag_arch;
```

## ROMs (Cont.)

**Example: 16 (Class)** *Repeat Example 15 using a LOOP statement.*

```
ARCHITECTURE loop_arch OF rom IS
    TYPE rm IS ARRAY (0 TO 2**n-1) OF unsigned (m-1 DOWNT0 0);
    SIGNAL word:  rm;
BEGIN
    memory:  PROCESS IS
BEGIN
    FOR index IN word'range LOOP
        word(index) <= to_unsigned(index*index, m);
    END LOOP;
    ASSERT FALSE REPORT "ROM init in loop_arch" SEVERITY note;
    LOOP
        WAIT ON enable, address;
        IF enable = '1' THEN
            data <= word(to_integer(address));
        ELSE
            data <= (OTHERS => 'Z');
        END IF;
    END LOOP;
END PROCESS memory;
END ARCHITECTURE loop_arch;
```

## ROMs (Cont.)

**Example: 17 (Class)** *Rewrite the architecture in Example 15 using a separate process without a sensitivity list to initialize the ROM.*

```
ARCHITECTURE init_process_arch OF rom IS
    TYPE rm IS ARRAY (0 TO 2**n-1) OF unsigned (m-1 DOWNT0 0);
    SIGNAL word:  rm;
    SIGNAL initialized:  boolean := false;
BEGIN
    init_wait_proc:  PROCESS IS
    BEGIN
        FOR index IN word'range LOOP
            word(index) <= to_unsigned(index*index, m);
        END LOOP;
        ASSERT FALSE REPORT "ROM init in init_wait_proc" SEVERITY note;
        initialized <= true;
        WAIT;
    END PROCESS init_wait_proc;

    :
```



## ROMs (Cont.)

### Example 17: (Cont.)

```
        :  
memory:  PROCESS (initialized, enable, address) IS  
BEGIN  
    IF initialized THEN  
        IF enable = '1' THEN  
            data <= word(to_integer(address));  
        ELSE  
            data <= (OTHERS => 'Z');  
        END IF;  
    END IF;  
END PROCESS memory;  
END ARCHITECTURE init_process_arch;
```

## ROMs (Cont.)

**Example: 18 (Class)** *Rewrite the initializing process in Example 17 using a sensitivity list.*

```

    :
init_sens_proc:  PROCESS (initialized) IS
BEGIN
    IF NOT initialized THEN
        FOR index IN word'range LOOP
            word(index) <= to_unsigned(index*index, m);
        END LOOP;
        ASSERT FALSE REPORT "ROM init in init_sens_proc" SEVERITY note;

        initialized <= true;
    END IF;
END PROCESS init_sens_proc;
    :

```

**Note:** This process will actually run twice. But, the ROM itself will be initialized only once.

## ROMs (Cont.)

**Example: 19 (Class)** *Repeat Example 15, initializing the ROM with a function.*

```
ARCHITECTURE funct_arch OF rom IS
  TYPE rm IS ARRAY (0 TO 2**n-1) OF unsigned (m-1 DOWNT0 0);
  FUNCTION rom_fill RETURN rm IS
    VARIABLE memory:  rm;
  BEGIN
    FOR index IN memory'range LOOP
      memory(index) := to_unsigned(index*index, m);
    END LOOP;
    ASSERT FALSE REPORT "ROM init in funct_arch" SEVERITY note;
    RETURN memory;
  END FUNCTION rom_fill;
  constant word:  rm := rom_fill;
BEGIN
  memory:  PROCESS (enable, address) IS BEGIN
    IF enable = '1' THEN
      data <= word(to_integer(address));
    ELSE
      data <= (OTHERS => 'Z');
    END IF;
  END PROCESS memory;
END ARCHITECTURE funct_arch;
```

## ROMs (Cont.)

**Example: 20 (Class)** *Rewrite the function in Example 19, initializing the ROM from a text file.*

```
LIBRARY ieee;
USE std.textio.ALL;
USE ieee.std_logic_textio.ALL;

:
:
IMPURE FUNCTION rom_fill RETURN rm IS
    VARIABLE memory:  rm;
    FILE f:  text OPEN READ_MODE IS "rom.txt";
    VARIABLE l:  line;
    VARIABLE read_word:  std_logic_vector (m-1 DOWNT0 0);
BEGIN
    FOR index IN memory'range LOOP
        readline (f, l);
        read (l, read_word); -- cannot read unsigned values from a file
        memory(index) := unsigned(read_word);
    END LOOP;
    ASSERT FALSE REPORT "ROM init in funct_arch & file" SEVERITY note;
    RETURN memory;
END FUNCTION rom_fill;
```

## ROMs (Cont.)

**Example: 21 (Class)** *Repeat Example 15, initializing the ROM using a generate statement.*

```
ARCHITECTURE gen_arch OF rom IS
    TYPE rm IS ARRAY (0 TO 2**n-1) OF unsigned (m-1 DOWNT0 0);
    SIGNAL word:  rm;
BEGIN
    contents:  FOR index IN word'range GENERATE
        word(index) <= to_unsigned(index*index, m);
    END GENERATE contents;


    data <=  word(to_integer(address)) WHEN enable = '1' ELSE
              (OTHERS => 'Z');
END ARCHITECTURE gen_arch;
```

# RAMs

**Example: 22 (Class)** *Show how to model an  $n$ -bit address,  $m$ -bit word size, dual-port RAM.*

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
ENTITY dual_port_ram IS
    GENERIC( n: positive := 4;
             m: positive := 4);
    PORT( r, w: IN std_logic;
          address_in: IN unsigned (n-1 DOWNTO 0);
          address_out: IN unsigned (n-1 DOWNTO 0);
          data_in: IN std_logic_vector (m-1 DOWNTO 0);
          data_out: OUT std_logic_vector (m-1 DOWNTO 0));
END ENTITY dual_port_ram;

:
```

 

## RAMs (Cont.)

### Example 22: (Cont.)

```

      :
      :
ARCHITECTURE behav OF dual_port_ram IS
BEGIN
    memory: PROCESS (r, w, address_in, address_out, data_in) IS
        TYPE rm IS ARRAY (0 TO 2**n-1) OF std_logic_vector (m-1 DOWNTO 0);
        VARIABLE word:  rm;
    BEGIN
        IF w = '1' THEN          -- write location in memory
            word(to_integer(address_in)) := data_in;
        END IF;


        IF r = '1' THEN          -- read location in memory
            data_out <= word(to_integer(address_out));
        END IF;
    END PROCESS memory;
END ARCHITECTURE behav;
```

## RAMs (Cont.)

 **Example: 23 (Class)** *Show how to model an  $n$ -bit address,  $m$ -bit word size, single-port RAM.*

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE ieee.numeric_std.ALL;
```

```
ENTITY single_port_ram IS  
  GENERIC( n: positive := 4;  
           m: positive := 4);  
  PORT( rw, enable: IN std_logic;  
        address: IN unsigned (n-1 DOWNTO 0);  
        data: INOUT std_logic_vector (m-1 DOWNTO 0));  
END ENTITY single_port_ram;  
  
:
```





## RAMs (Cont.)

### Example 23: (Cont.)

⋮

```
ARCHITECTURE behav OF single_port_ram IS BEGIN
  memory: PROCESS (rw, enable, address, data) IS
    TYPE rm IS ARRAY (0 TO 2**n-1) OF std_logic_vector (m-1 DOWNT0 0);
    VARIABLE word:  rm;
  BEGIN
    data <= (OTHERS => 'Z');
    IF enable = '1' THEN
      IF rw = '1' THEN          -- write location in memory
        word(to_integer(address)) := data;
      ELSE                      -- read location in memory
        data <= word(to_integer(address));
      END IF;
    END IF;
  END PROCESS memory;
END ARCHITECTURE behav;
```

**Example: 24 (Home)** *Explain why data is all driven to Z at the beginning of the process in Example 23.*